

# AC RC CIRCUITS

The term “AC” stands for “Alternating Current”, typically the 60 Hz power available from any North American electrical outlet.<sup>1</sup> A complete discussion of AC circuits must involve the “inertial” effect of **inductance**, but a useful introduction can be developed using only **capacitance**  $C$  and **resistance**  $R$ .

We begin by picturing a generic series- $RC$  circuit driven by a sinusoidal voltage  $\mathcal{E}(t) = \mathcal{E}_0 \cos(\omega t) = \Re e^{i\omega t}$ . It is convenient to use the complex form<sup>2</sup> for calculations; just remember that none of the actual physical quantities like current or voltage will actually have a measurable imaginary part.<sup>3</sup> The voltage amplitude  $\mathcal{E}_0$  is taken to be pure real.

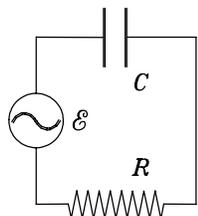


Figure 21.1 An  $RC$  circuit driven by an AC voltage.

## 21.1 The Differential Equation

Applying Kirchoff’s rule of single-valued potential around this loop, we have

$$\mathcal{E} - \frac{1}{C}Q - R\dot{Q} = 0. \quad (1)$$

When the AC power supply is first turned on, we might expect to see some complicated behaviour that eventually fades away, so that the circuit can settle down to the only plausible “steady-state” motion, namely for  $Q$  to oscillate at the same frequency as the driving voltage. We express this expectation as a **trial solution**:

$$Q(t) = Q_0 e^{i\omega t}. \quad (2)$$

Bearing in mind that the constant amplitude  $Q_0$  may not be entirely real, let’s see if this trial solution (2) “works” — *i.e.* satisfies the differential equation.

<sup>1</sup>In Europe and much of Asia the standard is 50 Hz.

<sup>2</sup>Here  $\Re$  signifies “the real part of” a complex quantity like  $e^{i\theta} = \cos\theta + i\sin\theta$ . The imaginary part is written (*e.g.*)  $\Im e^{i\theta} = \sin\theta$ .

<sup>3</sup>Let me know if you invent an imaginary voltmeter!

One motive for using the complex exponential form is that it is so easy to take derivatives: each time derivative of  $Q(t)$  just “pulls down” another factor of  $i\omega$ . Thus

$$\mathcal{E}_0 e^{i\omega t} - \frac{1}{C}Q_0 e^{i\omega t} - i\omega RQ_0 e^{i\omega t} = 0, \quad (3)$$

from which we can remove the common factor  $e^{i\omega t}$  and do a little algebra to obtain

$$Q_0 = \frac{\mathcal{E}_0/R}{1/RC + i\omega} = \frac{\mathcal{E}_0/R}{\lambda + i\omega} \quad (4)$$

where

$$\lambda \equiv \frac{1}{RC} \equiv \frac{1}{\tau}. \quad (5)$$

Now, the charge on a capacitor cannot be measured directly; what we usually want to know is the *current*  $I \equiv \dot{Q}$ . Since the entire time dependence of  $Q$  is in the factor  $e^{i\omega t}$ , we have trivially

$$I(t) = i\omega Q(t) = I_0 e^{i\omega t} \quad (6)$$

where

$$I_0 = i\omega Q_0 = \frac{i\omega \mathcal{E}_0/R}{\lambda + i\omega} = \frac{\mathcal{E}_0/R}{1 - i\lambda/\omega}. \quad (7)$$

Since everything we might want to know ( $\mathcal{E}$ ,  $Q$  and  $I$ ) has the same time dependence except for differences of *phase* encoded in the complex amplitudes  $Q_0$  and  $I_0$ , we can think in terms of an *effective resistance*  $R_{\text{eff}}$  such that

$$\mathcal{E} = IR_{\text{eff}} \quad \text{or} \quad R_{\text{eff}} = \frac{\mathcal{E}_0}{I_0}. \quad (8)$$

With a little more algebra we can write the effective resistance in the form

$$R_{\text{eff}} = R - iX_C \quad (9)$$

where

$$X_C \equiv \frac{1}{\omega C} \quad (10)$$

is the *capacitive reactance* of the circuit. This is a quantity that “act like” (and has the units of) a *resistance* — just like  $R$ , the first term in  $R_{\text{eff}}$ .

The *current* through the circuit cannot be different in different places (due to charge conservation) and follows the time dependence of the driving voltage but (because  $R_{\text{eff}}$  is generally complex) is not generally in *phase* with it, nor with the *voltage drop* across  $C$ :

$$\begin{aligned} -\Delta\mathcal{E}_R &= IR, & \text{but} \\ -\Delta\mathcal{E}_C &= -iIX_C. \end{aligned} \quad (11)$$

From Eqs. (9) and (11) one can easily deduce the *phase differences* between these voltages at any time (for example,  $t = \pi/\omega$ ) when  $\mathcal{E}$  has its maximum negative real value: the voltage drop across  $R$  will be real and positive (it is always exactly out of phase with the driving voltage) but the voltage drop across the capacitor will be in the negative imaginary direction — *i.e.* its real part will be zero at that instant.

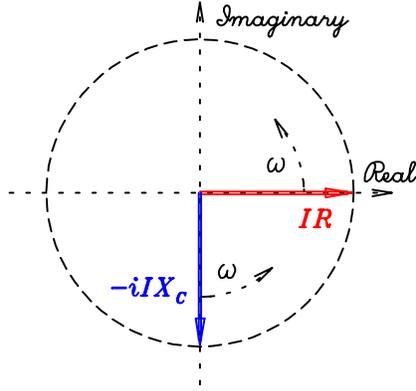


Figure 21.2 The “Phase Circle”.

A convenient way of looking at this is with the “Phase Circle” shown in Fig. 21.2, where the “directions” of the voltage drops in “complex phase space” are shown as vectors. Both voltage drops “rotate” in this “phase space” at a constant frequency  $\omega$  but their phase relationship is always preserved: namely, the voltage across the *capacitor lags* that across the resistor by an angle of  $\pi/2$ .<sup>4</sup> At any instant the actual, measurable value of any voltage is just its *real part*, *i.e.* the projection of its complex vector onto the real axis.

<sup>4</sup>There are many ways of remembering this phase relationship; I prefer to think of it this way: when the current starts flowing there is immediately a voltage drop across the resistor, but it takes a while to charge up the capacitor, so it *lags behind*. Use whatever works for you.

## 21.2 Power

From the point of view of the power supply,<sup>5</sup> the circuit is a “black box” that “resists” the applied voltage with a rather weird “back  $\mathcal{EMF}$ ”  $\mathcal{E}_{\text{back}}$  given by  $R_{\text{eff}}$  times the current  $I$ ;  $\mathcal{E}_{\text{back}}$  is given by the sum of both terms in Eq. (11) or the sum of the two vectors in Fig. 21.2. The *power* dissipated in the circuit is the product of the real part of the applied voltage<sup>6</sup> and the real part of the resultant current<sup>7</sup>

$$\begin{aligned} P(t) &= \Re \mathcal{E} \times \Re I = \Re (\mathcal{E}_0 e^{i\omega t}) \Re (I_0 e^{i\omega t}) \\ &= \mathcal{E}_0^2 \Re \left( \frac{1}{R_{\text{eff}}} \right) \cos^2(\omega t). \end{aligned} \quad (12)$$

which oscillates at a frequency  $2\omega$  between zero and its maximum value

$$P_{\text{max}} = \mathcal{E}_0^2 \Re \left( \frac{1}{R_{\text{eff}}} \right) \quad (13)$$

so that the *average power drain* is<sup>8</sup>

$$\langle P \rangle = \frac{1}{2} \mathcal{E}_0^2 \left[ \frac{R}{R^2 + X_C^2} \right]. \quad (14)$$

A little more algebra will yield the practical formula

$$\langle P \rangle = \mathcal{E}_{\text{rms}} I_{\text{rms}} \cos \phi \quad (15)$$

where  $\mathcal{E}_{\text{rms}} = \mathcal{E}_0/\sqrt{2}$ ,  $I_{\text{rms}}$  is the root-mean-square current in the circuit,

$$\cos \phi = \frac{R}{Z} \quad (16)$$

is the “*power factor*” of the  $RC$  circuit and

$$Z \equiv \sqrt{R^2 + X_C^2} \quad (17)$$

is the *impedance* of the circuit.<sup>9</sup>

This gets a lot more interesting when we add the “inertial” effects of **inductance** to our circuit. Stay tuned.

<sup>5</sup>Please forgive my anthropomorphization of circuit elements; these metaphors help me remember their “behaviour”.

<sup>6</sup>The imaginary voltage component doesn’t generate any power.

<sup>7</sup>Neither does the imaginary part of the current.

<sup>8</sup>I have used  $\frac{1}{x + iy} = \frac{x - iy}{x^2 + y^2}$  to obtain the real part of  $1/R_{\text{eff}}$ .

<sup>9</sup>Expressing the average power dissipation in this form allows one to think of an AC  $RC$  circuit the same way as a DC  $RC$  circuit with the *power factor* as a sort of “fudge factor”.